

## Experiment -1

**Aim:- Design all gates using VHDL.**

## 1. OR gate

**Code:-**

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_or is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );

end dee_or;

--}} End of automatically maintained section
```


architecture Behavioral of dee\_or is

begin

$$z \leq a \text{ or } b;$$

end Behavioral;

**Output:-**

 

## 2. AND gate

### Code:-

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_and is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );

end dee_and;

--}} End of automatically maintained section
```


architecture Behavioral of dee\_and is

begin

$z \leq a \text{ and } b;$

end Behavioral;

### Output:-

 

### 3. NOT gate

#### Code:-

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_not is

    port(

        a : in STD_LOGIC;

        z : out STD_LOGIC

    );

end dee_not;

--}} End of automatically maintained section
```


architecture Behavioral of dee\_not is

begin

```
z<= not a;
```

end Behavioral;

#### Output:-

 

#### 4. NAND gate

**Code:-**

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_nand is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );


end dee_nand;

--}} End of automatically maintained section
```

architecture Behavioral of dee\_nand is

```
begin
    z<= a nand b;
end Behavioral;
```

**Output:-**

 

## 5. NOR gate

### Code:-

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_nor is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );

end dee_nor;

--}} End of automatically maintained section
```


architecture Behavioral of dee\_nor is

begin

```
z<= a nor b;
```

end Behavioral;

### Output:-

 

## 6. EX-OR gate

### Code:-

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_exor is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );

end dee_exor;

--}} End of automatically maintained section
```


architecture Behavioral of dee\_exor is

begin

```
z <= a xor b;
```

end Behavioral;

### Output:-

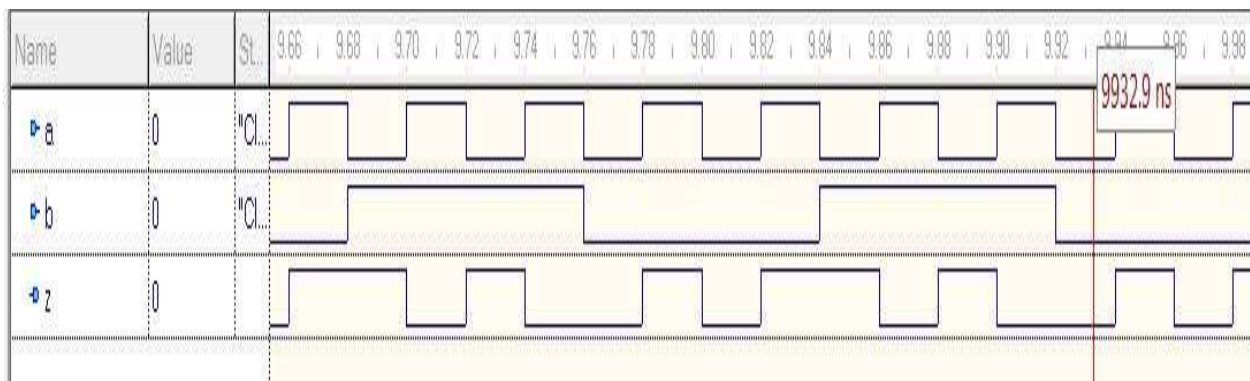

## 7. EX-NOR gate

**Code:-**

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_exnor is

    port(

        a : in STD_LOGIC;

        b : in STD_LOGIC;

        z : out STD_LOGIC

    );


end dee_exnor;

--}} End of automatically maintained section
```

architecture Behavioral of dee\_exnor is

```
begin
    z<= a xnor b;
end Behavioral;
```

**Output:-**

 

## Experiment – 2

**Aim :-** Write VHDL programs for the following circuits, check the wave forms and the hardware generated

- i) half adder
- ii) full adder

### 1. Half-adder

#### Code :-

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity \dee_half-adder\ is
```

```
    port(
```

```
        a : in STD_LOGIC;
```

```
        b : in STD_LOGIC;
```

```
        sum : out STD_LOGIC;
```

```
        carry : out STD_LOGIC
```

```
    );
```

```
end \dee_half-adder\;
```

```
--}} End of automatically maintained section
```

```
architecture Behavioral of \dee_half-adder\ is
```

```
begin
```


```
    sum<= a xor b;
```

```
    carry <= a and b;
```

```
end Behavioral;
```



## **Output :-**

 

## **2. Full-adder**

### **Code :-**

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity \dee_full-adder\ is
```

```
    port(
```

```
        a : in STD_LOGIC;
```

```
        b : in STD_LOGIC;
```

```
        ci : in STD_LOGIC;
```

```
        sum : out STD_LOGIC;
```

```
        cout : out STD_LOGIC
```

```
    );
```

```
end \dee_full-adder\;
```

```
--}} End of automatically maintained section
```

architecture Behavioral of \dee\_full-adder\ is


begin

sum<= a xor b xor ci;

cout <= (a and b) or (b and ci) or ( a and ci);

end Behavioral;

### **Output :-**

 

## Experiment – 3

**Aim :-** Write VHDL programs for the following circuits, check the wave forms and the hardware generated

- i) half subtractor
- ii) full subtractor

### 1. Half-subtractor

#### Code :-

```
library IEEE;

use IEEE.STD_LOGIC_1164.all;

entity dee_half_sub is

    port(    a : in STD_LOGIC;

            b : in STD_LOGIC;

            D : out STD_LOGIC;

            Bo : out STD_LOGIC

    );

end dee_half_sub;

--}} End of automatically maintained section

architecture Behavioral of dee_half_sub is


begin

    D<=a xor b;

    Bo<= (not a) and b;

end Behavioral;
```

#### Output :-

 

## 2. Full-subtractor

### Code :-

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity dee_full_sub is
```

```
    port( a : in STD_LOGIC;
```

```
          b : in STD_LOGIC;
```

```
          bi : in STD_LOGIC;
```

```
          D : out STD_LOGIC;
```

```
          Bo : out STD_LOGIC
```

```
    );
```

```
end dee_full_sub;
```

```
--}} End of automatically maintained section
```

```
architecture Behavioral of dee_full_sub is
```


```
begin
```

```
    D<= a xor b xor bi;
```

```
    Bo<= ((not a) and b) or ((not a) and bi) or (bi and b);
```

end Behavioral;

**Output :-**

 

## **Experiment – 4**

**AIM :-** Write a VHDL program for the converting bits in following ways and check the waveforms generated.

- 1.Binary to Gray
- 2.Gray to Binary

**CODE:-**

### **1. Binary to gray**

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity binary_gray is
    port(
        b0 : in STD_LOGIC;
        b1 : in STD_LOGIC;
        b2 : in STD_LOGIC;
        b3 : in STD_LOGIC;
        g0 : out STD_LOGIC;
        g1 : out STD_LOGIC;
        g2 : out STD_LOGIC;
        g3 : out STD_LOGIC
    );
end binary_gray;


--}} End of automatically maintained section

architecture behavioral of binary_gray is
begin

    g0<= b0;
    g1<=b0 xor b1;
    g2<=b1 xor b2;
    g3<= b2 xor b3;

end behavioral;
```

**OUTPUT :-**

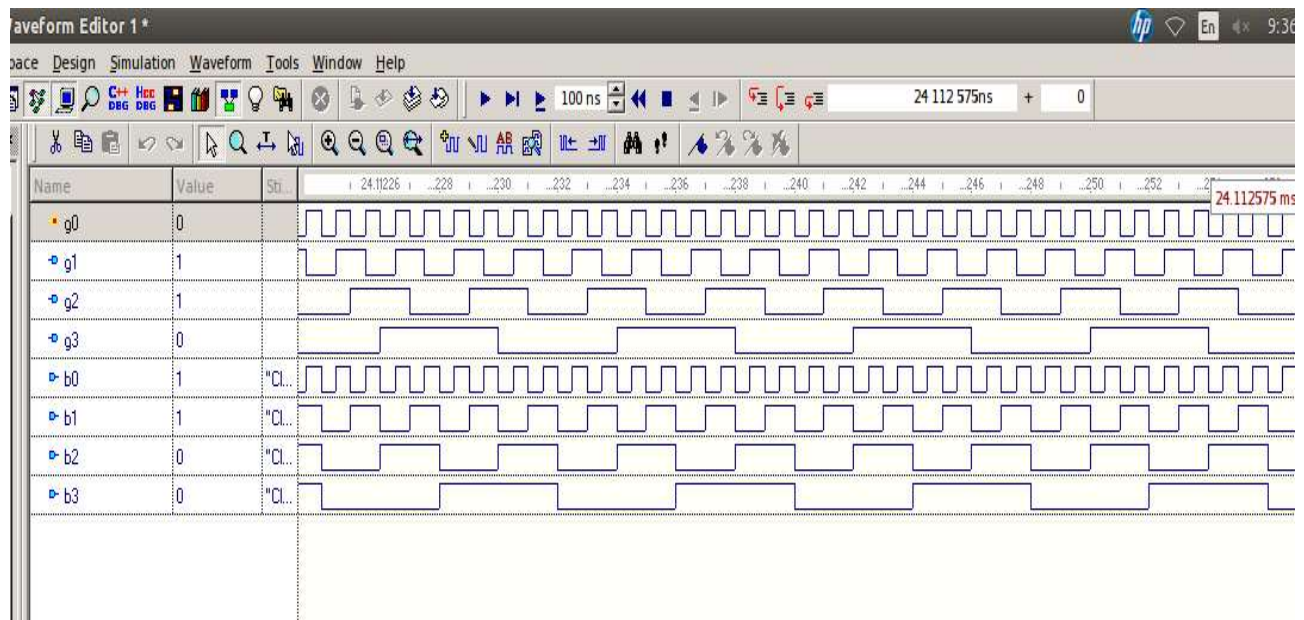

## 2.Gray to Binary

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity GRAY_BINARY is
    port(
        G0 : in STD_LOGIC;
        G1 : in STD_LOGIC;
        G2 : in STD_LOGIC;
        G3 : in STD_LOGIC;
        B0 : out STD_LOGIC;
        B1 : out STD_LOGIC;
        B2 : out STD_LOGIC;
        B3 : out STD_LOGIC
    );
end GRAY_BINARY;

--}} End of automatically maintained section

architecture BEHAVIORAL of GRAY_BINARY is
begin

    B0<=G0;
    B1<=B0 XOR G1;

```


```

B2<=B1 XOR G2;
B3<= B2 XOR G3;

```

end BEHAVIORAL;

## OUTPUT:-

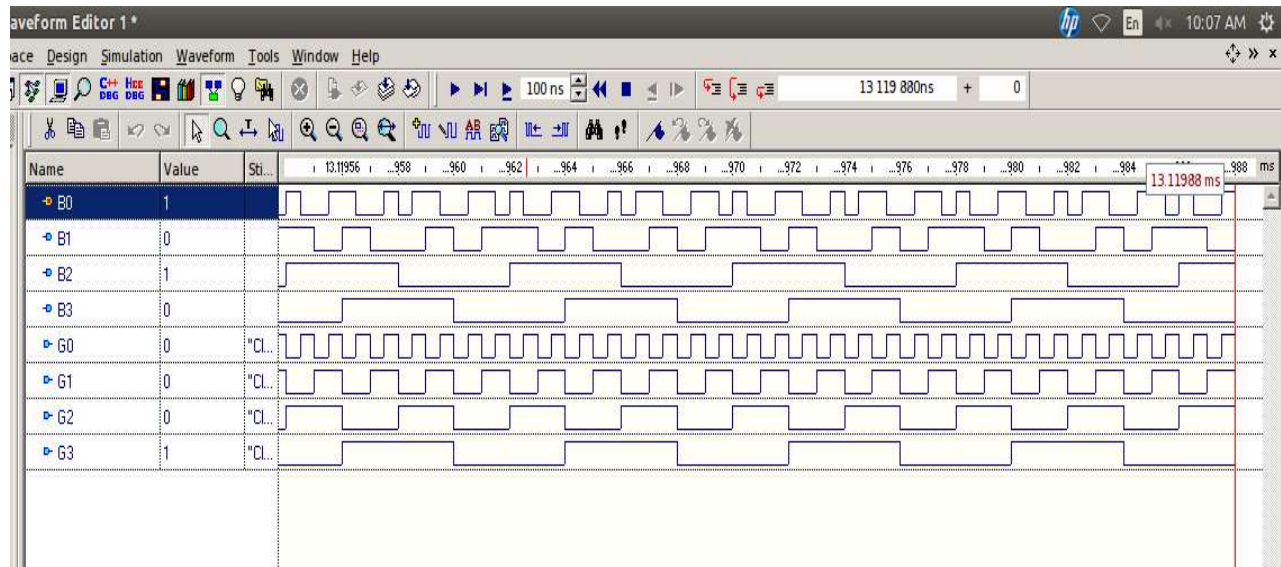



## Experiment – 5

**Aim :-** Write a VHDL program for a comparator and check the wave forms.

**Code:-**

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity comparator is
    port(
        a : in STD_LOGIC;
        b : in STD_LOGIC;
        y1 : out STD_LOGIC;           -- y1= (a>b)
        y2 : out STD_LOGIC;           -- y2= (a=b)
        y3 : out STD_LOGIC;           -- y3= (a<b)
    );
end comparator;

--}} End of automatically maintained section

architecture Behavioral of comparator is
begin
    process(a,b)
    begin
        if a='0' and b='0' then
            y1<='0';                  -- y1= (a>b)
            y2<='1';                  -- y2= (a=b)
            y3<='0';                  -- y3= (a<b)
        elsif a='0' and b='1' then
            y1<='0';
```

```

        y2<='0';

        y3<='1';

    elsif a='1' and b='0' then

        y1<='1';

        y2<='0';

        y3<='0';

    elsif a='1' and b='1' then

        y1<='0';

        y2<='1';

        y3<='0';

    else

        y1<='0';

        y2<='0';

        y3<='0';


    end if;

end process;

end Behavioral;

```

### **Output :-**

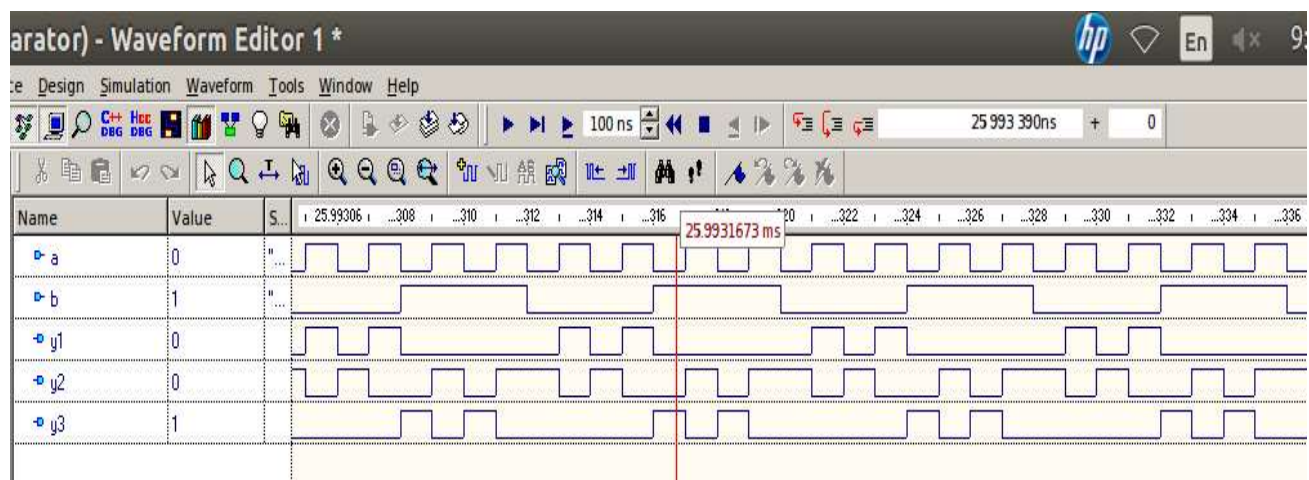

## Experiment – 6

**Aim :-** Write a VHDL program for BCD to 7 segment display and checks the waveform.

**Code:-**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity bcd_7seg is
Port ( b0,b1,b2,b3 : in STD_LOGIC;
a,b,c,d,e,f,g: out STD_LOGIC);
end bcd_7seg;


architecture Behavioral of bcd_7seg is

begin

a <= b0 OR b2 OR (b1 AND b3) OR (NOT b1 AND NOT b3);
b <= (NOT b1) OR (NOT b2 AND NOT b3) OR (b2 AND b3);
c <= b1 OR NOT b2 OR b3;
d <= (NOT b1 AND NOT b3) OR (b2 AND NOT b3) OR (b1 AND NOT b2 AND b3) OR (NOT b1 AND b2) OR
b0;
e <= (NOT b1 AND NOT b3) OR (b2 AND NOT b3);
f <= b0 OR (NOT b2 AND NOT b3) OR (b1 AND NOT b2) OR (b1 AND NOT b3);
g <= b0 OR (b1 AND NOT b2) OR ( NOT b1 AND b2) OR (b2 AND NOT b3);

end Behavioral;
```

**Output :-**

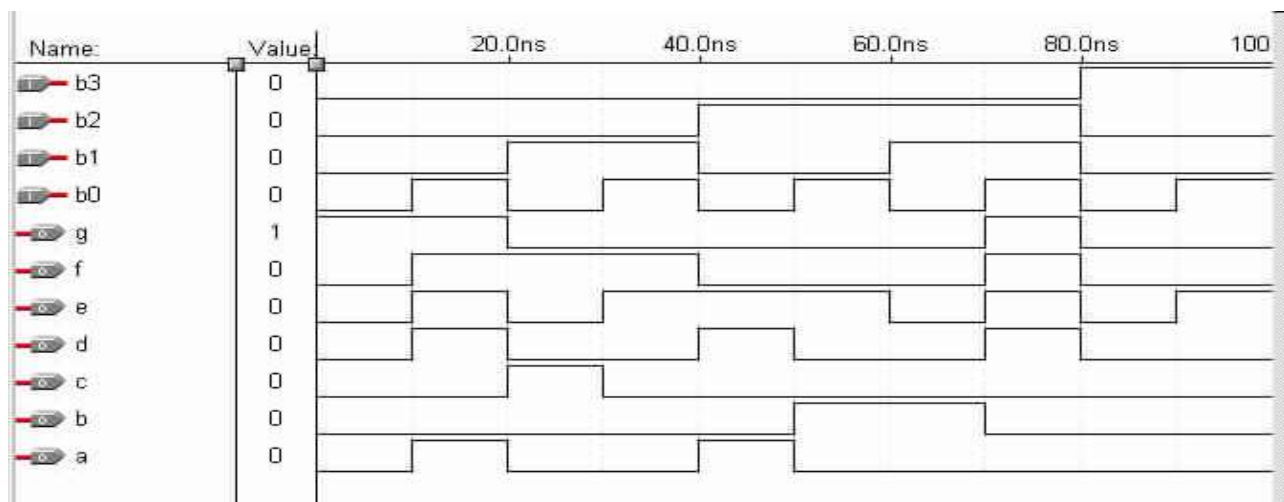

## Experiment – 7

**Aim :-** Write a VHDL program for a 4 bit multiplexer and check the wave forms.

**Code:-** Using selective statement

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.all;
```

```
entity selective_mux4 is
```

```
    port(
```

```
        sel : in STD_LOGIC_VECTOR(1 DOWNTO 0);
```

```
        a : in STD_LOGIC;
```

```
        b : in STD_LOGIC;
```

```
        c : in STD_LOGIC;
```

```
        d : in STD_LOGIC;
```

```
        z : out STD_LOGIC
```

```
    );
```

```
end selective_mux4;
```

```
--}} End of automatically maintained section
```

```
architecture Dataflow of selective_mux4 is
```

```
begin
```

```
    with sel select
```

**Output :-**



```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity mux4 is
    port(
        i0 : in STD_LOGIC;
        i1 : in STD_LOGIC;
```

```

        i2 : in STD_LOGIC;

        i3 : in STD_LOGIC;

        s0 : in STD_LOGIC;

        s1 : in STD_LOGIC;

        z : out STD_LOGIC

    );

end mux4;

--}} End of automatically maintained section

architecture Dataflow of mux4 is


begin

    z<=( (not s0 and not s1) and i0 )or ((not s0 and s1) and i1) or ( ( s0 and not s1) and i2) or
    ( ( s0 and s1) and i3);

end Dataflow;

```

## **Output :-**

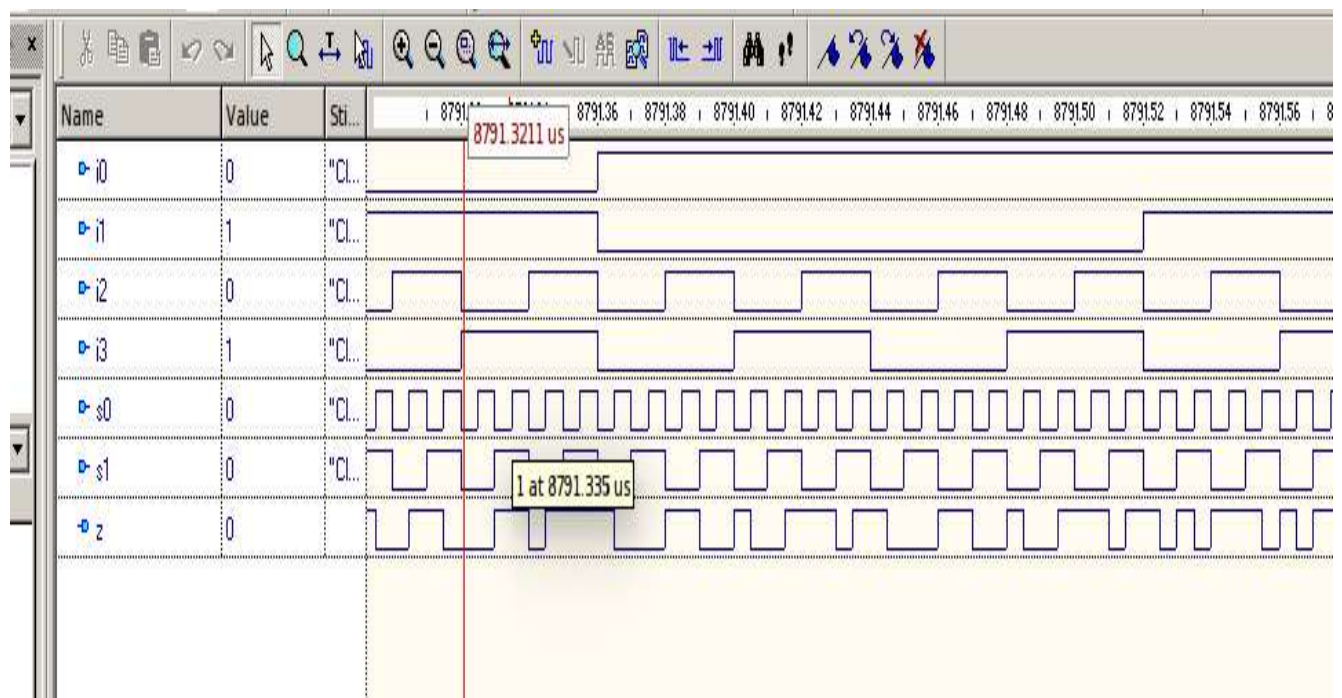

## Experiment – 8

**AIM :-** Write a VHDL program for a 3x8 decoder and check the waveforms.

### Code:-

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity deco3_8 is
    port(
        D : in STD_LOGIC_VECTOR(0 TO 2);
        O : out STD_LOGIC_VECTOR( 0 TO 7)
    );
end deco3_8;

--}} End of automatically maintained section


architecture selective of deco3_8 is

begin

    with D select
    O<= "10000000" when "000",
    "01000000" when "001",
    "00100000" when "010",
    "00010000" when "011",
    "00001000" when "100",
    "00000100" when "101",
    "00000010" when "110",
    "00000001" when "111",
    "00000000" when others;

end selective;
```

Output:-

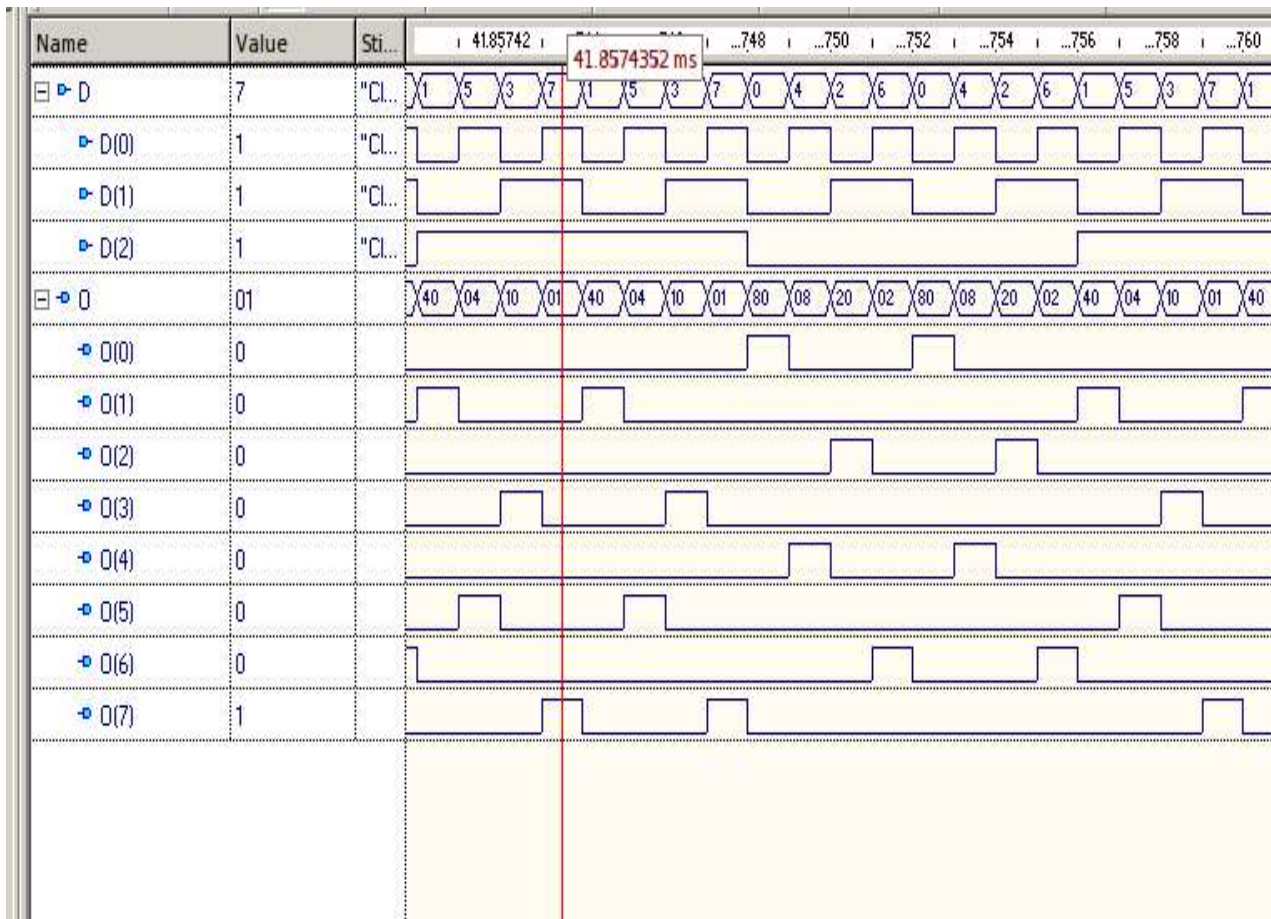



## Experiment – 9

**AIM :-** Write a VHDL program for T-flipflop and check the waveforms.

### Code:-

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity T_flipflop is
    port(
        p : in STD_LOGIC;
        c : in STD_LOGIC;
        clk : in STD_LOGIC;
        t : in STD_LOGIC;
        q : inout STD_LOGIC;
        qb : inout STD_LOGIC
    );
end T_flipflop;

--}} End of automatically maintained section

architecture behavioral of T_flipflop is
begin

    process(clk,p,c)
    begin
        if (p='0') then
            q<='1';
            qb<='0';
        elsif (c='0') then
            q<='0';
            qb<='1';
        elsif(p='0' and c='0') then
            q<='X';
            qb<='X';
        elsif(clk='0') then
            if (t='1') then
                q<=not q;
            end if;
        end if;
    end process;
end;
```

```

        qb<=not qb;
    else
        q<=q;
        qb<=not q;
    end if;
end if;
end process;

```

end behavioral;

## Output:-

