

## Experiment - 9.

Aim: Write test bench for full adder circuit with VHDL code.

Software: MODEL SIM.


Theory: A test bench is a model that is used to exercise and verify the correctness of a hardware model. A test bench is needed for three main purposes.

- To generate stimulus for simulation (waveforms)
- To apply this stimulus to the entity under test and to monitor the output responses.
- To compare output responses with expected known values.

Steps to write a test bench:

- The entity port list is always empty.
- Under the architecture, all the components are declared for the under unit test (UUT).
- Inputs are declared & initialized to zero along with O/Ps.
- For sequential circuits, clock period is defined too.
- UUT is initialized and process for stimulus is written for sequential designs, process for clock is called.

Circuit Diagram:

 

Full adder.

## BOOLEAN EXPRESSIONS:

$C_{in}$	$B$	$A$	$S$	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
0	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = A \oplus B \oplus C$$

$$C_{out} = AB + BC_{in} + AC_{in}$$

Result:- Test bench for full adder circuit was written and implemented in VHDL.

# Codes

## Full Adder vhdl code

```
library ieee;
use ieee.std_logic_1164.all;
entity full_adder is
    port (
        a : in  std_logic;
        b : in  std_logic;
        ci : in  std_logic;
        s : out std_logic;
        co : out std_logic);
end;
architecture ADDER of full_adder is
begin
    s <= ((not a) and (not b) and ci) or (a and (not b) and (not ci)) or ((not
        a) and b and (not ci)) or (a and b and ci);
    co <= (a and b) or (b and ci) or (a and ci) ;
end;
```

## Full Adder VHDL testbench

```
library ieee;
use ieee.std_logic_1164.all;
entity adder_tb is
end adder_tb;

architecture ADDER of adder_tb is
    component full_adder is
        port (
            a : in  std_logic;
            b : in  std_logic;
            ci : in  std_logic;
            s : out std_logic;
            co : out std_logic);
    end component;
    signal input  : std_logic_vector(2 downto 0);
    signal output : std_logic_vector(1 downto 0);
begin
    uut: full_adder port map (
        a => input(2),
        b => input(1),
        ci => input(0),
        s => output(0),
        co => output(1)
    );

    stim_proc: process
    begin
        input <= "000"; wait for 10 ns; assert output = "00" report "0+0+0 failed";
        input <= "001"; wait for 10 ns; assert output = "01" report "0+0+1 failed";
        input <= "010"; wait for 10 ns; assert output = "01" report "0+1+0 failed";
        input <= "011"; wait for 10 ns; assert output = "10" report "0+1+1 failed";
        input <= "100"; wait for 10 ns; assert output = "01" report "1+0+0 failed";
        input <= "101"; wait for 10 ns; assert output = "10" report "1+0+1 failed";
        input <= "110"; wait for 10 ns; assert output = "10" report "1+1+0 failed";
        input <= "111"; wait for 10 ns; assert output = "11" report "1+1+1 failed";
        report "Full adder testbench finished";
        wait;
    end process;
end;
```

## Output

 


Figure 1: BASIC GATES

## Result

Testbench for full adder circuit was written and implemented in VHDL