

Program Code:

SR Flip Flop:

```
library ieee;
use ieee.std_logic_1164.all;

entity srff is
    port(S, R, CLK: in std_logic;
         Q, Qbar: out std_logic);
end srff;

architecture arch_srff of srff is
    begin

        process(CLK)
            begin
                if (S /= R) and rising_edge(CLK) then
                    Q <= S;
                    Qbar <= R;

                elsif (S = '1') and rising_edge(CLK) then
                    Q <= 'Z';
                    Qbar <= 'Z';
                end if;

            end process;
        end arch_srff;
```

D Flip Flop:

```
library ieee;
use ieee.std_logic_1164.all;

entity dff is
    port(D, CLK: in std_logic;
         Q, Qbar: out std_logic);
end dff;

architecture arch_dff of dff is
    begin

        process(CLK)
            begin
                if rising_edge(CLK) then
                    Q <= D;
                    Qbar <= not D;

                end if;
            end process;
        end arch_dff;
```

JK Flip Flop:

```
library ieee;
use ieee.std_logic_1164.all;

entity jkff is
    port(J, K, CLK: in std_logic;
         Q, Qbar: inout std_logic);
end jkff;

architecture arch_jkff of jkff is
    begin

        process(CLK)
            begin
                if (J /= K) and rising_edge(CLK) then
                    Q <= J;
                    Qbar <= K;

                elsif (J = '1') and rising_edge(CLK) then
                    Q <= not Q;
                    Qbar <= not Qbar;
                end if;

            end process;
        end arch_jkff;
```

T Flip Flop:

```
library ieee;
use ieee.std_logic_1164.all;

entity tff is
    port(T, CLK: in std_logic;
         Q, Qbar: inout bit);
end tff;


architecture arch_tff of tff is
    begin

        process(CLK)
            begin
                if (T = '1') and rising_edge(CLK) then
                    Q <= not Q;
                    Qbar <= not Qbar;
                end if;


            end process;
        end arch_tff;
```

OUTPUT:


SR Flip Flop

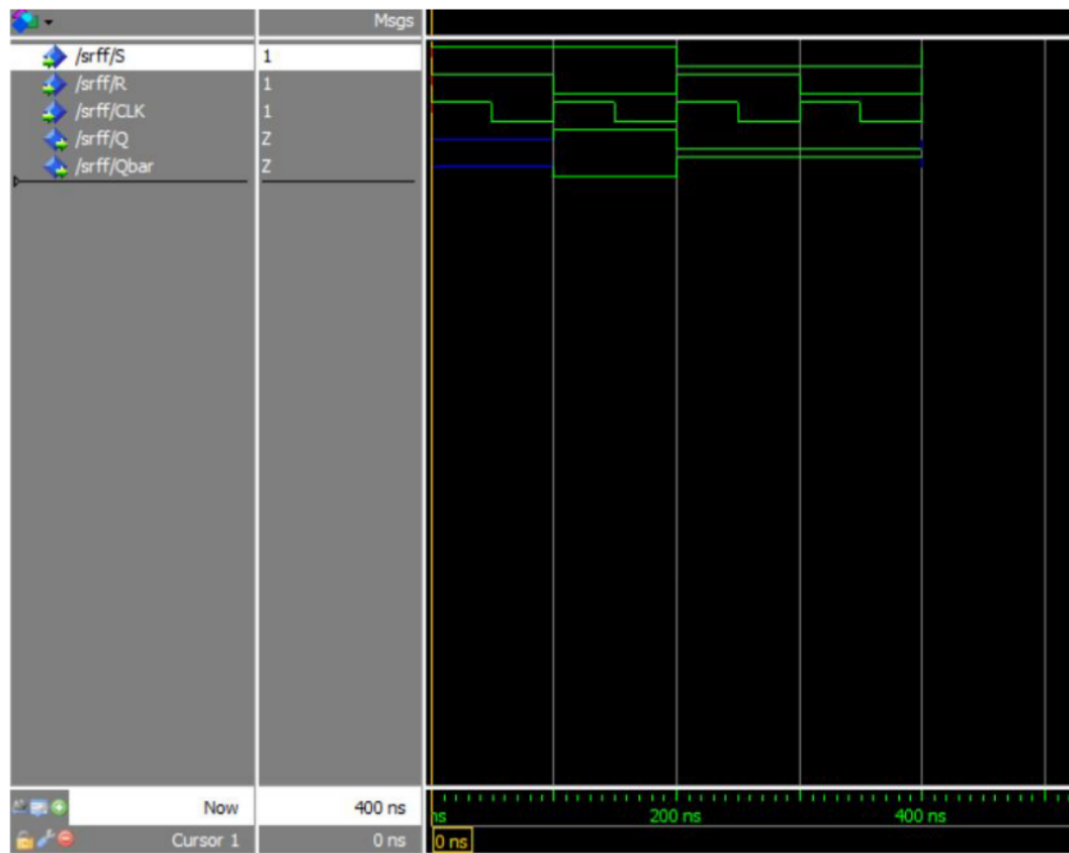


D Flip Flop

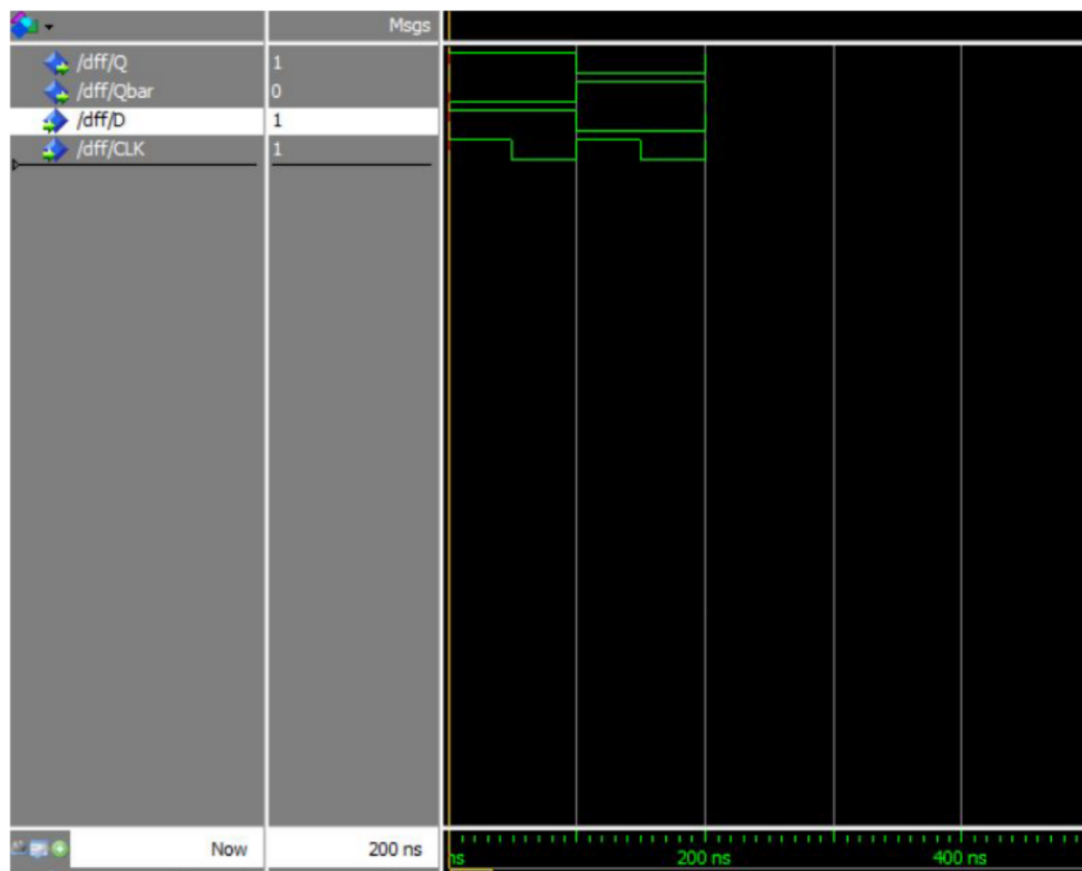

JK Flip Flop

 

T Flip Flop

 

Result: Hence we have studied and programmed the following flip flops in vhdl.