

Experiment-4

Aim: To design and implement following:


1. 4:1 mux using 2:1 mux
2. 8:1 mux using 4:1 mux
3. 16:1 mux using 4:1 mux
4. Full adder using HA
5. Full Subtractor using HS

Software Used:- ModelSim

Theory:- 4:1 Mux Using 2:1 Mux:

A 4:1 mux consists of four data inputs lines as I_0 to I_3 , 2 select lines as S_0 and S_1 . And single output Y . When S_0 & $S_1 = 0$ then Y is I_0 , if Y is I_1 if $S_0 = 1$, & $S_1 = 0$ & so on.

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

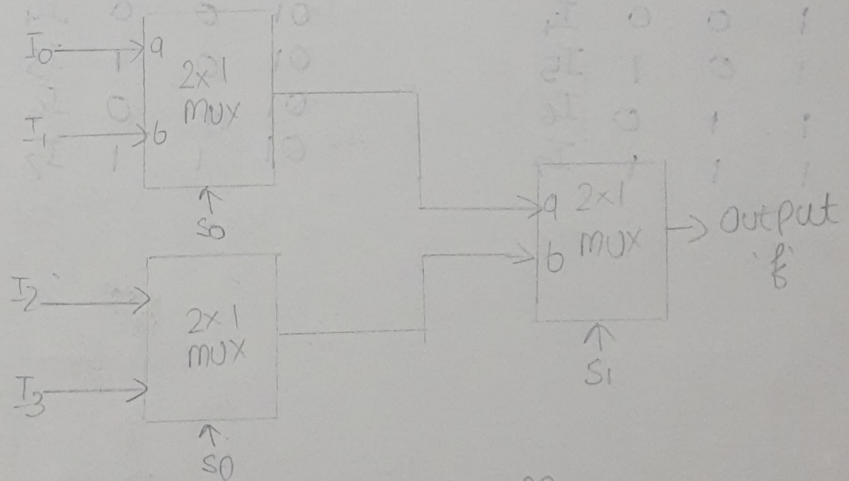

4:1 MUX using 2:1 MUX

The truth table for 2:1 mux using 4:1 mux is.

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

8:1 mux using 4:1 mux

In this configuration, 2 4:1 mux & 1 2:1 mux is required.
The two multiplexers in first stage in order to get 8 data inputs
and 2:1 mux is second stage.

11 Using Or gate & 4:1 Mux


It contains 2 4:1 mux which will take 8 inputs & the outputs
of first stage is passed through the or gate to or gate to
get the output

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


2 4:1 mux & 2:1 mux

E	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
01	0	0	I_4
01	0	1	I_5
01	1	0	I_6
01	1	1	I_7

2 4:1 mux & OR gate

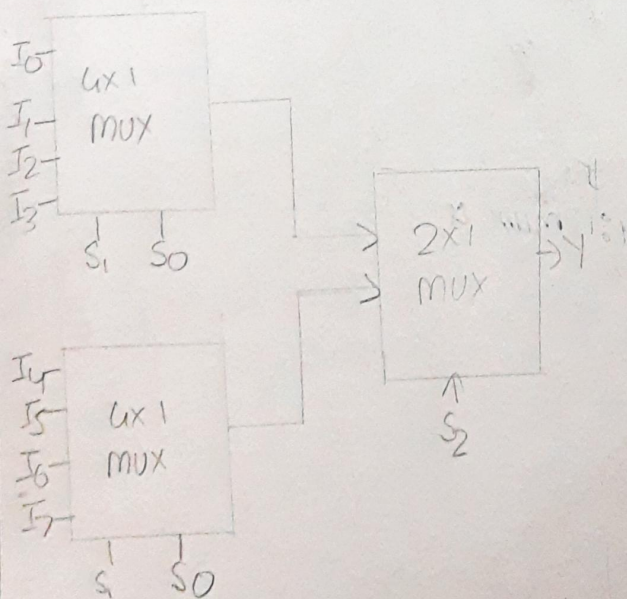

8:1 mux using 4:1 &
2:1 mux

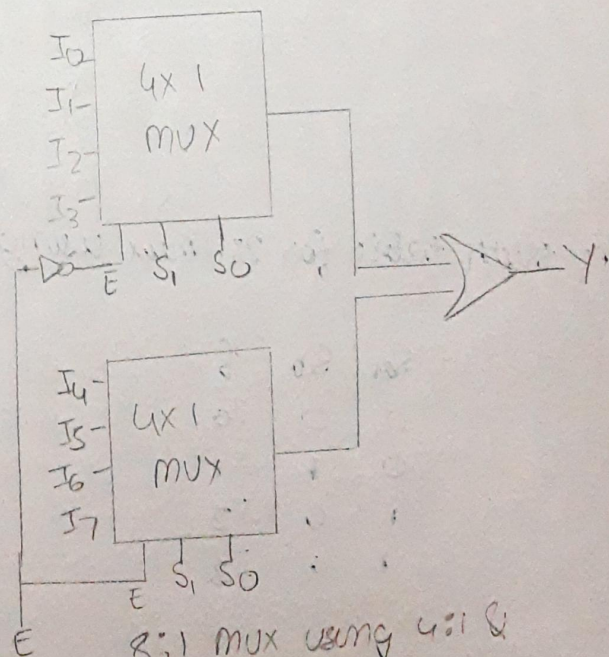


8:1 mux using 4:1 &
OR gate

3. 16:1 Mux Using 4:1 Mux:

It contains 16 input lines & 4 select lines. 5 '4x1' mux are used out of which 4 '4x1' mux are used to get 16 input lines and the output of the mux & fed to another 4x1 mux to get desired output.

S_0	S_1	S_2	S_3	Y
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}
1	1	1	0	I_{14}
1	1	1	1	I_{15}

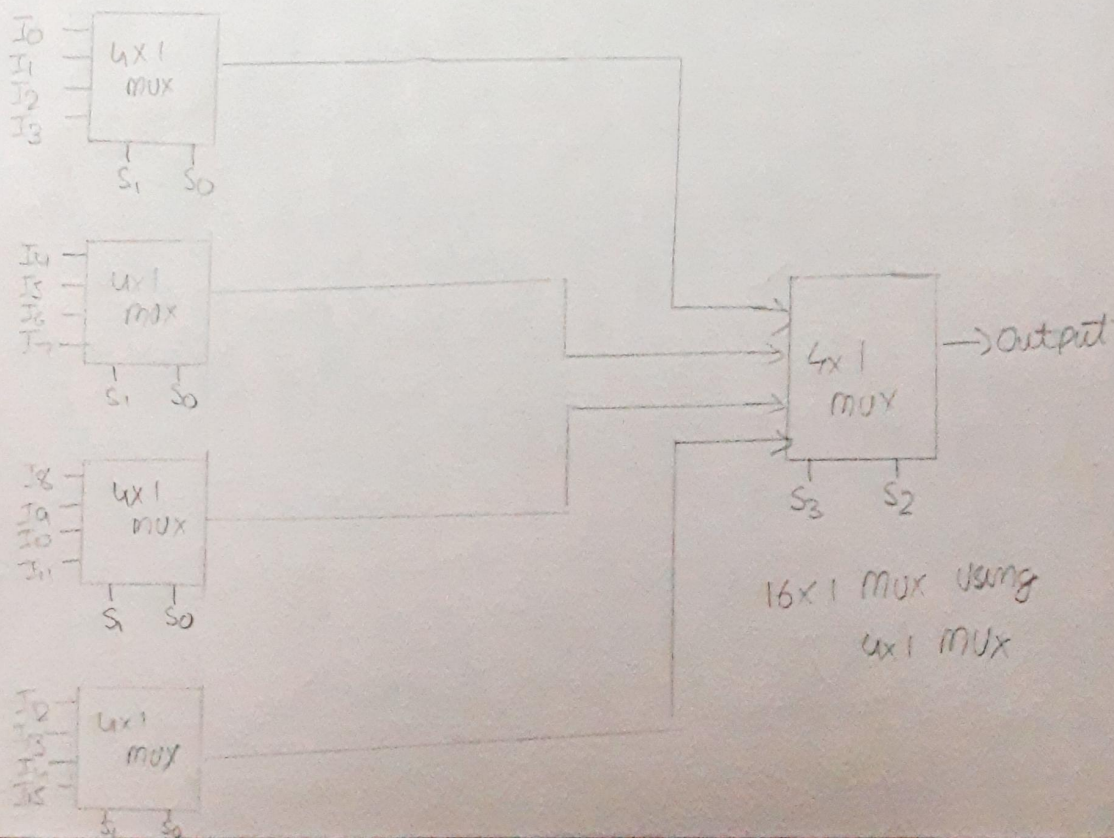


1. Full Adder Using Half Adder :- Full adder is adder which adds 3 input and produces two output. The first two inputs are A and B & third input carry C_{in} . The output is Sum & Cout. To implement full adder 2 half adder & 2 or gate is required.


Full Subtractor using Half Subtractor :- Full subtractor is subtractor which subtracts 3 inputs and produces two output. The first two inputs are A and B and third input borrow as input. The output is B out & difference. To implement full sub 2 half sub & or gate is required.

A	B	C_{in}	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	B_{in}	Diff	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

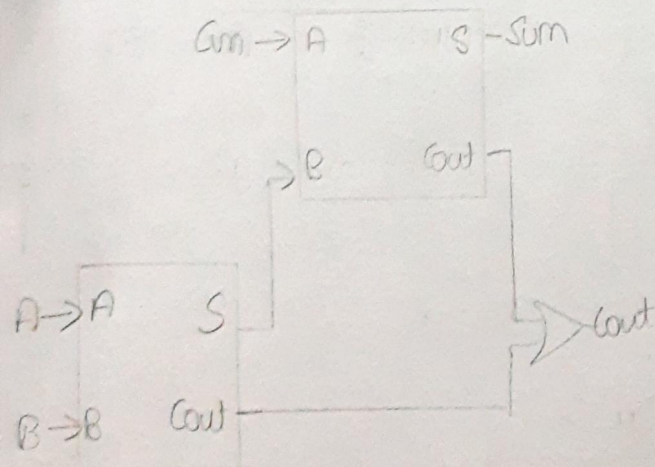

Full adder using Half adders.

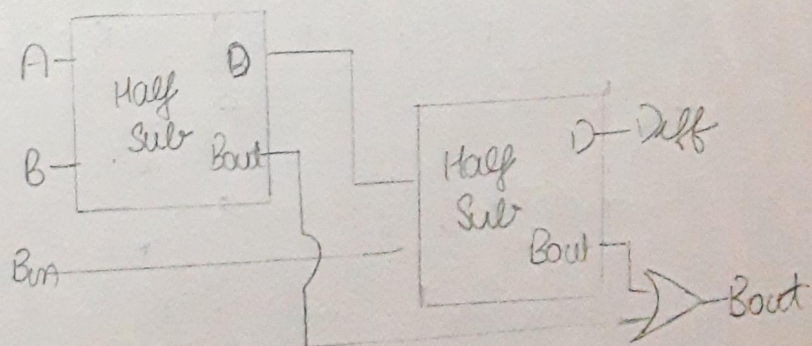

Full Subtractor using Half Subtractor.

Codes

1. 4:1 Mux using 2:1 Mux

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux4_1 is
port(
    A,B,C,D : in STD_LOGIC;
    S0,S1: in STD_LOGIC;
    Z: out STD_LOGIC
);
end mux4_1;

architecture smsa of mux4_1 is
component mux2_1
port(
    A,B : in STD_LOGIC;
    S: in STD_LOGIC;
    Z: out STD_LOGIC
);
end component;

signal temp1, temp2: std_logic;
begin
    m1: mux2_1 port map(A,B,S0,temp1);
    m2: mux2_1 port map(C,D,S0,temp2);
    m3: mux2_1 port map(temp1,temp2,S1,Z);
end smsa;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_1 is
port(
    A,B:in STD_LOGIC;
    S:in STD_LOGIC;
    Z:out STD_LOGIC
);
end mux2_1;

architecture sms of mux2_1 is
begin
    with S select
        Z<= A when '0',
        B when others;
end sms;
```

2. 8:1 Mux using 2:1 Mux and 4:1 Mux

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux8_1 is
port(
    A,B,C,D,E,F,G,H : in STD_LOGIC;
    S2,S1,S0: in STD_LOGIC;
    Z1: out STD_LOGIC
);
end mux8_1;

architecture smsa of mux8_1 is
    component mux2_1
    port(
        A,B:in STD_LOGIC;
        S2: in STD_LOGIC;
        Z: out STD_LOGIC
    );
    end component;

    component mux4_1
    port(
        A,B,C,D : in STD_LOGIC;
        S0,S1: in STD_LOGIC;
        Z: out STD_LOGIC
    );
    end component;

    signal temp1, temp2: std_logic;
begin
    m1: mux4_1 port map(A,B,C,D,S0,S1,temp1);
    m2: mux4_1 port map(E,F,G,H,S0,S1,temp2);
    m3: mux2_1 port map(temp1,temp2,S2,Z1);

end smsa;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux4_1 is
port(
    A,B,C,D : in STD_LOGIC;
    S0,S1 : in STD_LOGIC;
    Z : out STD_LOGIC
);
end mux4_1;

architecture sms of mux4_1 is
begin
    process (A,B,C,D,S0,S1) is
    begin
        if (S0 ='0' and S1 = '0') then
```

```

        Z <= A;
    elsif (S0 ='1' and S1 = '0') then
        Z <= B;
    elsif (S0 ='0' and S1 = '1') then
        Z <= C;
    else
        Z <= D;
    end if;
end process;
end sms;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2_1 is
port(
    A,B:in STD_LOGIC;
    S2:in STD_LOGIC;
    Z:out STD_LOGIC
);
end mux2_1;

architecture sms of mux2_1 is
begin
    with S2 select
        Z<= A when '0',
        B when others;
end sms;

```

3. 8:1 Mux using 4:1 mux and OR gate

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux8_1 is
port(
    A : in STD_LOGIC_VECTOR(7 downto 0);
    S: in STD_LOGIC_VECTOR(1 downto 0);
    E:in STD_LOGIC;
    Z1: out STD_LOGIC
);
end mux8_1;

architecture smsb of mux8_1 is
component orgate
    port(
        A,B:in STD_LOGIC;
        Z: out STD_LOGIC
    );
end component;

component multiplexer_4_1
    port(
        A : in STD_LOGIC_VECTOR(3 downto 0);
        S : in STD_LOGIC_VECTOR(1 downto 0);
        E:in STD_LOGIC;
        Z: out STD_LOGIC);
end component;
signal temp1, temp2,C: std_logic;
begin
    C<=not(E);
    m1: multiplexer_4_1 port map(A(3 downto 0),S,C,temp1);
    m2: multiplexer_4_1 port map(A(7 downto 4),S,E,temp2);
    m3: orgate port map(temp1,temp2,Z1);
end smsb;

library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity multiplexer_4_1 is
port(
    A : in STD_LOGIC_VECTOR(3 downto 0);
    S : in STD_LOGIC_VECTOR(1 downto 0);
    E:in STD_LOGIC;
    Z : out STD_LOGIC
);
end multiplexer_4_1;

architecture multiplexer4_1_arc of multiplexer_4_1 is
begin
    with S select
        Z <= A(0) and E when "00" ,
        A(1) and E when "01" ,
        A(2) and E when "10" ,
```



```
        A(3) and E when others;  
end multiplexer4_1_arc;
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity orgate is  
port(  
    A,B:in STD_LOGIC;  
    Z:out STD_LOGIC  
);  
end orgate;
```

```
architecture sms of orgate is  
begin  
    Z<=A or B;  
end sms;
```

4. 16:1 Mux using 4:1 Mux

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux16_1 is
    port(
        A : in STD_LOGIC_VECTOR(15 downto 0);
        S : in STD_LOGIC_VECTOR( 3 downto 0);
        Z1: out STD_LOGIC
    );
end mux16_1;

architecture smsb of mux16_1 is
    component multiplexer_4_1
        port(
            A : in STD_LOGIC_VECTOR( 3 downto 0);
            S : in STD_LOGIC_VECTOR( 1 downto 0);
            Z : out STD_LOGIC
        );
    end component;

    signal temp: STD_LOGIC_VECTOR(3 downto 0);
begin
    m1: multiplexer_4_1 port map( A(3 downto 0), S(1 downto 0), temp(0));
    m2: multiplexer_4_1 port map( A(7 downto 4), S(1 downto 0), temp(1));
    m3: multiplexer_4_1 port map( A(11 downto 8), S(1 downto 0), temp(2));
    m4: multiplexer_4_1 port map( A(15 downto 12), S(1 downto 0), temp(3));
    m5: multiplexer_4_1 port map(temp, S(3 downto 2), Z1);
end smsb;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity multiplexer_4_1 is
    port(
        A : in STD_LOGIC_VECTOR( 3 downto 0);
        S : in STD_LOGIC_VECTOR(1 downto 0);
        Z : out STD_LOGIC
    );
end multiplexer_4_1;

architecture multiplexer4_1_arc of multiplexer_4_1 is
begin
    with S select
        Z <= A(0) when "00",
            A(1) when "01",
            A(2) when "10",
            A(3) when others;
end multiplexer4_1_arc;
```

5. Full Adder using Half Adder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fulladder is
port(
A : in STD_LOGIC;
B: in STD_LOGIC;
C: in STD_LOGIC;
S:out STD_LOGIC;
CA: out STD_LOGIC
);
end fulladder;

architecture smsb of fulladder is
component orgate
port( A,B:in STD_LOGIC;
Z: out STD_LOGIC);
end component;

component half_adder
port( a : in STD_LOGIC;
b: in STD_LOGIC;
sum:out STD_LOGIC;
carry: out STD_LOGIC);
end component;

signal sum1,carry1,carry2: std_logic;
begin
m1: half_adder port map(A,B,sum1,carry1);
m2: half_adder port map(C,sum1,S,carry2);
m3: orgate port map(carry1,carry2,CA);

end smsb;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity half_adder is
    port(a,b:in STD_LOGIC; sum,carry:out STD_LOGIC);
end half_adder;

architecture halfadder of half_adder is
begin
    sum<= a xor b;
    carry <= a and b;
end halfadder;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity orgate is
port(A,B:in STD_LOGIC;
Z : out STD_LOGIC);
```



```

end orgate;
architecture sms of orgate is
begin
    Z <= A or B;
end sms;

```

6. Full Subtractor using Half Subtractor

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fullsubtractor is
port(
A : in STD_LOGIC;
B: in STD_LOGIC;
C: in STD_LOGIC;
D:out STD_LOGIC;
BO: out STD_LOGIC
);
end fullsubtractor;

architecture smsb of fullsubtractor is
    component orgate
        port( A,B:in STD_LOGIC;
            Z : out STD_LOGIC);
    end component;

    component half_subtractor
        port( a: in STD_LOGIC;
            b: in STD_LOGIC;
            diff : out STD_LOGIC;
            borrow: out STD_LOGIC);
    end component;

    signal sum1,carry1,carry2: std_logic;
begin
    m1: half_subtractor port map(A,B,sum1,carry1);
    m2: half_subtractor port map(C,sum1,D,carry2);
    m3: half_subtractor port map(carry1, carry2, BO);
end smsb;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity half_subtractor is
    port(a,b:in STD_LOGIC; diff,borrow:out STD_LOGIC);
end half_subtractor;
architecture halfsubtractor of half_subtractor is
begin
    diff <= a xor b;
    borrow <= not(a) and b;
end halfsubtractor;

```

Outputs

1. 4:1 Mux using 2:1 Mux

 


Figure 1: 4:1 Mux Using 2:1 Mux

2. 8:1 Mux using 2:1 Mux and 4:1 Mux

 


Figure 2: 8:1 Mux using 2:1 Mux and 4:1 Mux

3. 8:1 mux using 4:1 mux and or gate

 


Figure 3: 8:1 mux using 4:1 mux and or gate

4. 16:1 Mux using 4:1 Mux

 


Figure 4: 16:1 Mux using 4:1 Mux

5. Full Adder using Half Adder

 


Figure 5: Full Adder using Half Adder

6. Full Subtractor using Half Subtractor

 


Figure 6: Full Subtractor using Half Subtractor