

Experiment-4

Aim: To design and implement following:


1. 4:1 mux using 2:1 mux
2. 8:1 mux using 4:1 mux
3. 16:1 mux using 4:1 mux
4. Full adder using HA
5. Full Subtractor using HS

Software Used: - ModelSim

Theory: 4:1 Mux Using 2:1 Mux:

A 4:1 mux consists of four data inputs lines as I_0 to I_3 , 2 select lines as S_0 and S_1 . And single output Y . When S_0 & $S_1 = 0$ then Y is I_0 , if $S_0 = 1$, & $S_1 = 0$ & so on.

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

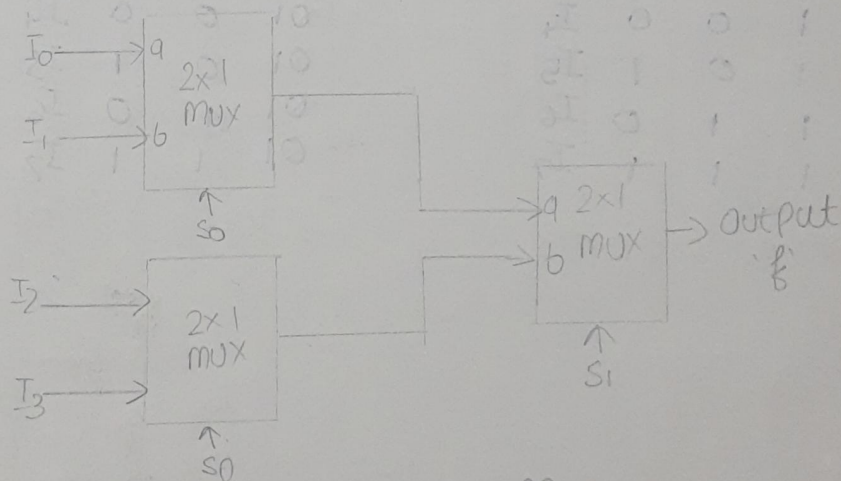

4:1 MUX using 2:1 MUX

The truth table for 2:1 mux using 4:1 mux is.

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

8:1 mux using 4:1 mux

In this configuration, 2 4:1 mux & 1 2:1 mux is required.
The two multiplexers in first stage in order to get 8 data inputs
and 2:1 mux is second stage.

11 Using Or gate & 4:1 Mux


It contains 2 4:1 mux which will take 8 inputs & the outputs
of first stage is passed through the or gate to or gate to
get the output

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


2 4:1 mux & 2:1 mux

E	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
01	0	0	I_4
01	0	1	I_5
01	1	0	I_6
01	1	1	I_7

2 4:1 mux & OR gate

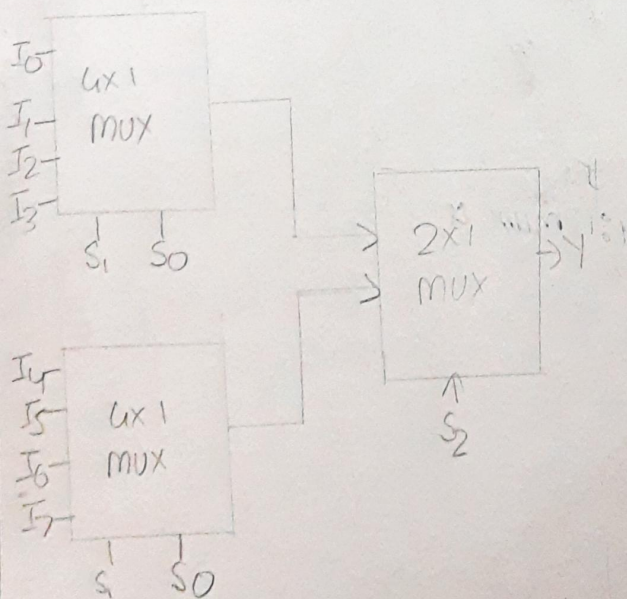

8:1 mux using 4:1 & 2:1 mux

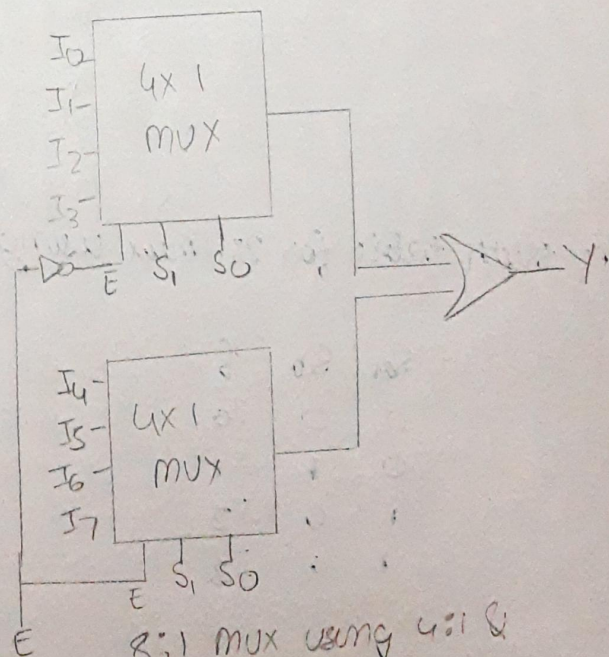


8:1 mux using 4:1 & OR gate

3. 16:1 Mux Using 4:1 Mux:

It contains 16 input lines & 4 select lines. 5 '4x1' mux are used out of which 4 '4x1' mux are used to get 16 input lines and the output of the mux & fed to another 4x1 mux to get desired output.

S_0	S_1	S_2	S_3	Y
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}
1	1	1	0	I_{14}
1	1	1	1	I_{15}

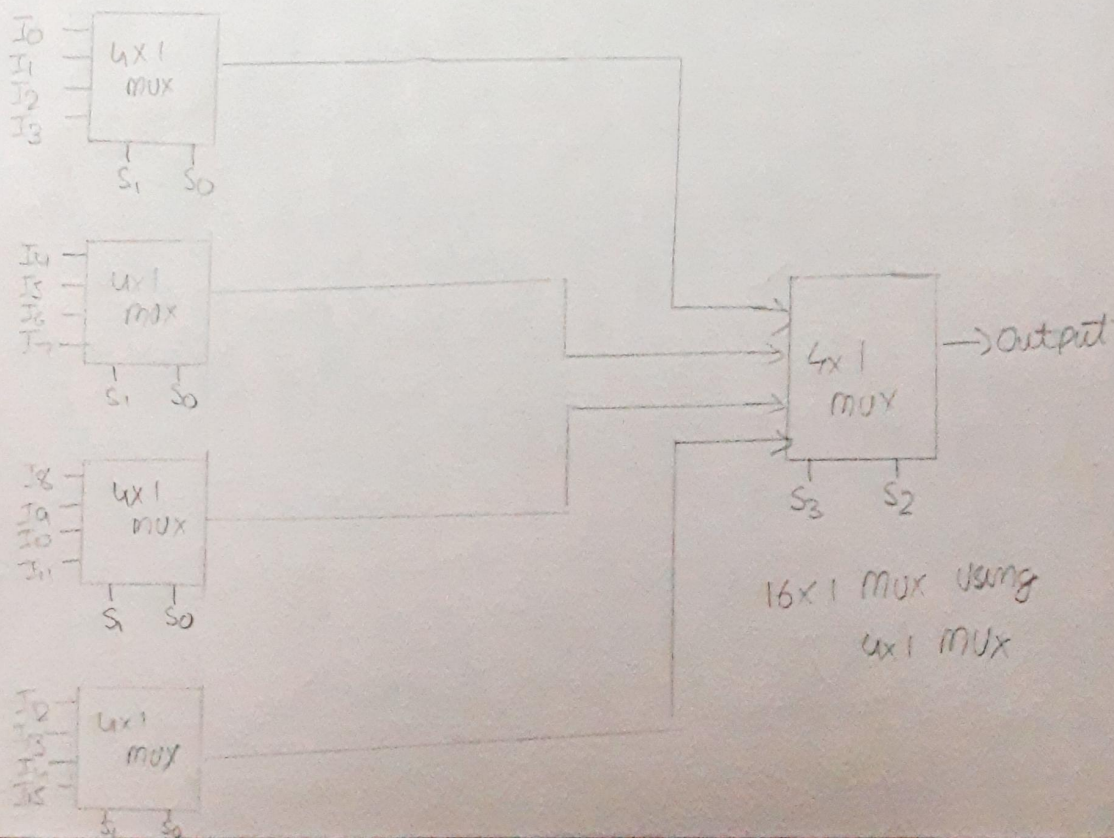


1. Full Adder Using Half Adder:- Full adder is adder which adds 3 input and produces two output. The first two inputs are A and B & third input carry C_{in} . The output is Sum & Cout. To implement full adder 2 half adder & 2 or gate is required.


Full Subtractor using Half Subtractor:- Full subtractor is subtractor which subtracts 3 inputs and produces two output. The first two inputs are A and B and third input borrow as input. The output is B out & difference. To implement full sub 2 half sub & or gate is required.

A	B	C_{in}	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A	B	B_{in}	Diff	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

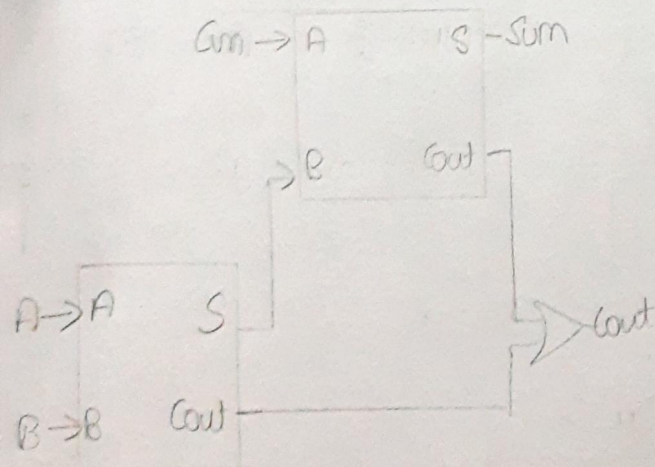

Full adder using Half adders.

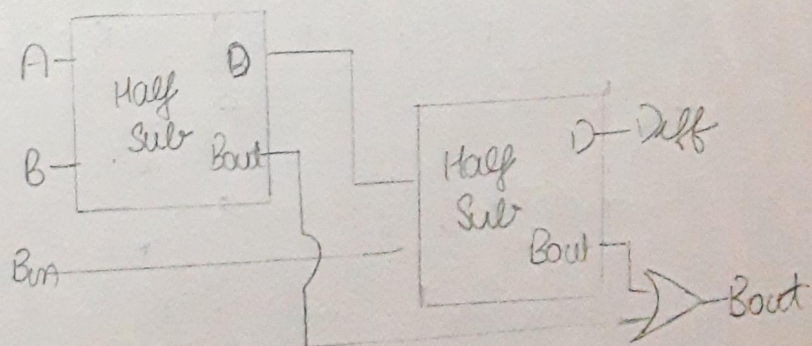

Full Subtractor using Half Subtractor.